 


CPE 233: Computer Design and Assembly Language Programming

HW #1:


DAC using Pulse-Width Modulation with RC Filter

By: Roee Landesman and Amir Hashemizad



<https://www.youtube.com/watch?v=1kDXINdvWHk&feature=youtu.be>


Black Box Block Diagram

 

Behavior Description

A pulse-width modulator controls the average output voltage of a microcontroller using a clock-divider. The component essentially determines the width of each pulse by translating a switch's value into binary and keeping the pulse high for that binary value. There is a simple counter in the clock-divider that increments on each rising edge. This entire PWM was then connected to a low-filter which allowed us to translate the sinusoidal wave into a square wave, effectively making a digital-to-analog convertor (DAC).

Structural Design

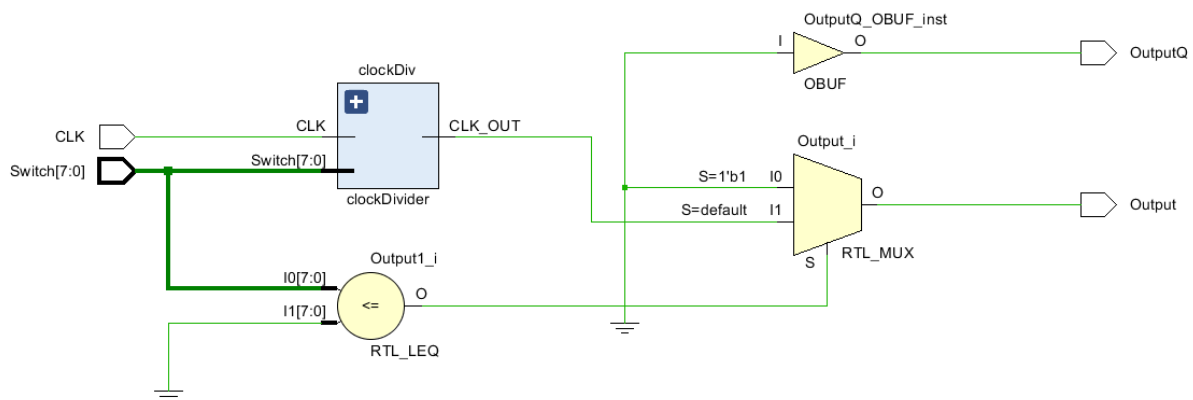

Specification

According to the schematic that we drew, the component should be able to work on any sized clock speed. We created an 8-bit DAC which means we have up to 256 unique voltage partitions; depending on the voltage of the hardware itself, determines the resolution of the converted analog signal. Additionally, since we are using the Basys3 FPGA, the PWM DAC is limited to a clock speed of 100 MHz, which means that the rising edge comes every 10 nanoseconds. The RC low-pass filter was built using a 1.6kOhm resistor and 100 nF capacitor to provide adequate time for the RC circuit to respond to the incoming rising edges.

VHDL Source Code

Main:

```
-----  
-- Engineer: Amir Hashemizad and Roei Landesman  
-- Create Date: 01/21/2018  
-- Module Name: HW1project_module - Behavioral  
-- Project Name: HW1  
-- Target Devices: Basys3 Board  
-- Revision 0.01 - File Created  
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
entity project_module is  
    Port ( Switch : in STD_LOGIC_VECTOR(7 downto 0);  
          CLK      : in STD_LOGIC;  
          OutputQ  : out STD_LOGIC;  
          Output   : out STD_LOGIC);  
end project_module;  
  
architecture Behavioral of project_module is  
  
    component clockDivider  
        port(  
            CLK : in std_logic;  
            Switch : in std_logic_vector(7 downto 0);  
            CLK_OUT : out std_logic);  
    end component;  
  
    signal OUT_TEMP : std_logic;  
  
begin  
  
    clockDiv: clockDivider port map(  
        CLK => CLK, Switch => Switch, CLK_OUT => OUT_TEMP);
```

```

process
Begin
    if (Switch <= "00000000") then
        Output <= '0';
    else
        Output <= OUT_TEMP;
    end if;
    OutputQ <= '0';
end process;

end Behavioral;

```

Clock Divider:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.all;

entity clockDivider is
    Port ( CLK : in STD_LOGIC;
          Switch : in STD_LOGIC_VECTOR(7 downto 0);
          CLK_OUT : out STD_LOGIC);
end clockDivider;

architecture Behavioral of clockDivider is

    signal TEMP_CLK : std_logic := '1';

begin

    process(CLK)
        variable count : integer := 0;
    begin
        if (rising_edge(CLK)) then
            if (count = to_integer(unsigned(Switch))) then
                TEMP_CLK <= '0';
            end if;
            if (count = 255) then
                TEMP_CLK <= '1';
                count := 0;
            end if;
            count := count + 1;
        end if;
    end process;

    CLK_OUT <= TEMP_CLK;

end Behavioral;

```

Example Use Code

The following RAT Assembly code utilizes the PWM DAC with RC Low filter that we built in order to create a triangle wave. This wave starts with a V_{rms} of 1.65 Volts and then increases and decreases from there up to 255.

```
.EQU PWM_PORT = 0x42

.CSEG
.ORG 0x20

MAIN: MOV    R0, 0x7F
UP:   OUT    R0, PWM_PORT
      ADD    R0, 0x01
      CMP    R0, 0xFF
      BREQ   DOWN
      BRN    UP
DOWN: OUT    R0, PWM_PORT
      SUB    R0, 0x01
      CMP    R0, 0x7F
      BREQ   UP
      BRN    DOWN
```